

CET3136 – Logic Devices Programming

Spring 2025

Experiment 9

Test Benches, BCD Counters, and Real-Time Clock

Performed By:

Anthony Paul Sevarino

Submitted to:

Prof. Ashley Evans

**Department of Electrical & Computer Engineering Technology (ECET)
School of Engineering, Technology, and Advanced Manufacturing (ETAM)
Valencia College**

Date Submitted

03/27/2025

Introduction

The intent of this lab is to create three distinct projects which each demonstrate a fundamental understanding of intermediate VHDL topics, those being test benches of clock-based systems, multi-digit BCD counters, and the implementation of various concepts into creating a real-world use-case project, in this case as a real-time clock. The commonality between each of the components to this experiment is the use of the clock, which on the MAX10 development board operates at 50MHz. Understanding of the seven-segment HEX displays is also vital to properly representing the logic derived in all parts of the lab. This study also uses a previously completed lab8B which acts as the system to be tested against in part A. ModelSim Altera will be used to create the functional simulation required for analysis in testbenching for part A.

LIST OF EQUIPMENT/PARTS/COMPONENTS/SOFTWARE

- DE10-Lite MAX-10 Dev Board
- USB 2.0 Type B Cable
- Windows Desktop
- Quartus FPGA Design Software

PROCEDURE / DISCUSSION

Part A – The Test Bench

This part of the study uses Lab8B to create a testbench against a system which utilizes a clock. Thus, an artificial clock must be generated in order to mimic the behavior of the actual clock on the development board.

Code Explanation Part A

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity testbench_eight_bit_counter is
6 end testbench_eight_bit_counter;
7
8 architecture behavior of testbench_eight_bit_counter is
9     signal enable_tb, clock_tb, clear_bar_tb : std_logic;
10     signal q_out_tb : std_logic_vector(7 downto 0);
11     signal hex1_tb, hex0_tb : std_logic_vector(6 downto 0);
12     constant period : time := 100 ns;
13
14     --Clock generation
15     procedure clk_gen (signal clock_tb : out std_logic) is
16         constant period : time := 100 ns;
17     begin
18         while true loop
19             clock_tb <= '0';
20             wait for period/2;
21             clock_tb <= '1';
22             wait for period/2;
23         end loop;
24     end procedure;
25
26 begin
27     --unit under test
28     uut : entity work.eightbitcounter
29     port map (
30         enable => enable_tb,
31         clock => clock_tb,
32         clear_bar => clear_bar_tb,
33         q_out => q_out_tb
34     );
35
36     --testbenching
37     tb : process
38     begin
39         --throw reset and unthrow enable
40         clear_bar_tb <= '0';
41         enable_tb <= '0';
42         wait for period; -- Let reset be active for one clock period
43
44         --throw reset
45         clear_bar_tb <= '1';
46         wait for period;
47
48         --throw enable
49         enable_tb <= '1';
50
51         --now check counts from 0 to 63
52         for i in 0 to 63 loop
53             wait until rising_edge(clock_tb); --wait for clock
54             assert q_out_tb = std_logic_vector(to_unsigned(i, 8))
55             report "testbench failed at: " & integer'image(i) & Integer'image(to_integer(unsigned(q_out_tb)))
56             error;
57         end loop;
58     end process;
59
60 end behavior;
```

Figure 1 - Completed Code for Part A

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity testbench_eight_bit_counter is
end testbench_eight_bit_counter;

architecture behavior of testbench_eight_bit_counter is
    signal enable_tb, clock_tb, clear_bar_tb: std_logic;
    signal q_out_tb : std_logic_vector(7 downto 0);
    signal hex1_tb, hex0_tb : std_logic_vector(6 downto 0);
    constant period : time := 100 ns;

    --clock generation
    procedure clk_gen (signal clock_tb : out std_logic) is
        constant period : time := 100 ns;
        begin
            while true loop
                clock_tb <= '0';
                wait for period/2;
                clock_tb <= '1';
                wait for period/2;
            end loop;
        end procedure;

begin
    --unit under test
    UUT : entity work.eightbitcounter
        port map (
            enable => enable_tb,
            clock  => clock_tb,
            clear_bar => clear_bar_tb,
            q_out  => q_out_tb
        );

    --testbenching
    tb : process
    begin
        --throw reset and unthrow enable
        clear_bar_tb <= '0';
        enable_tb  <= '0';
        wait for period; -- let reset be active for one clock period

        --unthrow reset
        clear_bar_tb <= '1';
        wait for period;

        --throw enable
        enable_tb <= '1';

        --now check counts from 0 to 63
        for i in 0 to 63 loop
            wait until rising_edge(clock_tb); --wait for clock

```

```

        assert q_out_tb = std_logic_vector(to_unsigned(i, 8))
        report "Testbench failed at: " & integer'image(i) & integer'image(to_integer(unsigned(q_out_tb))) &
std_logic'image(clear_bar_tb) & std_logic'image(enable_tb) severity error;
    end loop;
end process;

end behavior;

```

The entity portion contains no information, as it is a testbench and will substitute signals for all inputs and outputs of the circuit.

The architecture generates an artificial clock which will run indefinitely, independent of the requirements of the specific system (in this case running to 64). A *unit under test* block is created to attach the tested inputs and outputs to their testbench equivalents. Then, the testbench process tests against numerous cases, starting with clear on and enable off, then waiting for a clock period. Then, clear is disabled while enable is thrown. Finally, the *q_out* result can be checked iteratively through 64 repetitions. Each time, if the count is not matched by the UDT, which is asserted, then a report is given to the console with the respective iteration, value attachment, clear state, and enable state. Note that the part 8B experiment used to demonstrate this testbench was completed unsuccessfully and therefore throws various errors in testbenching.

There is no block diagram for this section of the study, as it is a testbench and not ported to a board nor assigned pins.

Part B – The 3-digit BCD Counter

This part of the lab requires for the construction of a 3-digit BCD counter, meaning each digit must count to *1001* in binary, or 9 in decimal. Thus, a simple binary counter is insufficient for completing this. Note that only a single value is used for the BCD while managing to break it into 3 components to be logically separated in the system.

Code Explanation Part B

```

4 architecture behavior of threedigbcdcounter is
5
6     signal clk_spread : integer range 0 to 49999999 := 0; -- 50MHz means 50 million cycles per second
7     signal bcdval : unsigned(11 downto 0) := "000000000000"; -- 12-bit BCD value
8
9 begin
10
11     process(input_clock, reset)
12     begin
13         if reset = '1' then
14             clk_spread <= 0;
15             bcdval <= "000000000000";
16         elsif rising_edge(input_clock) then
17             if clk_spread = 49999999 then --once clock reaches 1 second, reset clock and increment BCD
18                 clk_spread <= 0;
19                 if count_enable = '1' then
20                     if bcdval(3 downto 0) = "1001" then --first overflow
21                         bcdval(3 downto 0) <= "0000";
22                     if bcdval(7 downto 4) = "1001" then --second overflow
23                         bcdval(7 downto 4) <= "0000";
24                     if bcdval(11 downto 8) = "1001" then --third overflow
25                         bcdval(11 downto 8) <= "0000";
26                     else
27                         bcdval(11 downto 8) <= bcdval(11 downto 8) + 1;
28                     end if;
29                 else
30                     bcdval(7 downto 4) <= bcdval(7 downto 4) + 1;
31                 end if;
32             else
33                 bcdval(3 downto 0) <= bcdval(3 downto 0) + 1;
34             end if;
35         end if;
36         clk_spread <= clk_spread + 1;
37     end if;
38 end process;
39
40 process(output_enable)
41 begin
42     if output_enable = '1' then
43         --hex display conversions
44         case to_integer(bcdval(3 downto 0)) is
45             when 0 => hex0 <= "1000000";
46             when 1 => hex0 <= "1111001";
47             when 2 => hex0 <= "0100100";
48             when 3 => hex0 <= "0110000";
49             when 4 => hex0 <= "0011001";
50             when 5 => hex0 <= "0010010";
51             when 6 => hex0 <= "0000010";
52             when 7 => hex0 <= "1111000";
53             when 8 => hex0 <= "0000000";
54             when 9 => hex0 <= "0010000";
55             when others => hex0 <= "1111111";
56         end case;
57
58         case to_integer(bcdval(7 downto 4)) is
59             when 0 => hex1 <= "1000000";
60             when 1 => hex1 <= "1111001";
61             when 2 => hex1 <= "0100100";
62             when 3 => hex1 <= "0110000";
63             when 4 => hex1 <= "0011001";
64             when 5 => hex1 <= "0010010";
65             when 6 => hex1 <= "0000010";
66             when 7 => hex1 <= "1111000";
67             when 8 => hex1 <= "0000000";
68             when 9 => hex1 <= "0010000";
69             when others => hex1 <= "1111111";
70         end case;
71
72         case to_integer(bcdval(11 downto 8)) is
73             when 0 => hex2 <= "1000000";
74             when 1 => hex2 <= "1111001";
75             when 2 => hex2 <= "0100100";
76             when 3 => hex2 <= "0110000";
77             when 4 => hex2 <= "0011001";
78             when 5 => hex2 <= "0010010";
79             when 6 => hex2 <= "0000010";
80             when 7 => hex2 <= "1111000";
81             when 8 => hex2 <= "0000000";
82             when 9 => hex2 <= "0010000";
83             when others => hex2 <= "1111111";
84         end case;
85     else
86         hex0 <= "1111111";
87         hex1 <= "1111111";
88         hex2 <= "1111111";
89     end if;
90 end process;
91
92 end behavior;
93 end threedigbcdcounter;

```

Figure 2 - Completed Code for Part B

-----MAIN BLOCK-----

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity threedigbcdcounter is
port (
    input_clock, reset, count_enable, output_enable : in std_logic;
    hex0, hex1, hex2 : out std_logic_vector(6 downto 0)
);
end threedigbcdcounter;

architecture behavior of threedigbcdcounter is

```

```

signal clk_spread : integer range 0 to 49999999 := 0;      -- 50MHz means 50 million cycles per second
signal bcdVal : unsigned(11 downto 0) := "000000000000"; -- 12-bit BCD value

begin

    process(input_clock, reset)
    begin
        if reset = '1' then
            clk_spread <= 0;
            bcdVal <= "000000000000";
        elsif rising_edge(input_clock) then
            if clk_spread = 49999999 then --once clock reaches 1 second, reset clock and
increment BCD
                clk_spread <= 0;
                if count_enable = '1' then
                    if bcdVal(3 downto 0) = "1001" then --first overflow
                        bcdVal(3 downto 0) <= "0000";
                        if bcdVal(7 downto 4) = "1001" then --second overflow
                            bcdVal(7 downto 4) <= "0000";
                            if bcdVal(11 downto 8) = "1001" then --third
overflow
                                bcdVal(11 downto 8) <= "0000";
                                else
                                    bcdVal(11 downto 8) <= bcdVal(11 downto
8) + 1;
                                end if;
                            else
                                bcdVal(7 downto 4) <= bcdVal(7 downto 4) + 1;
                                end if;
                        else
                            bcdVal(3 downto 0) <= bcdVal(3 downto 0) + 1;
                            end if;
                        end if;
                    end if;
                else
                    clk_spread <= clk_spread + 1;
                end if;
            end if;
        end process;

        process(output_enable)
        begin
            if output_enable = '1' then
                --hex display conversions
                case to_integer(bcdVal(3 downto 0)) is
                    when 0 => hex0 <= "1000000";
                    when 1 => hex0 <= "1111001";
                    when 2 => hex0 <= "0100100";
                    when 3 => hex0 <= "0110000";
                    when 4 => hex0 <= "0011001";
                    when 5 => hex0 <= "0010010";
                    when 6 => hex0 <= "0000010";
                    when 7 => hex0 <= "1111000";
                    when 8 => hex0 <= "0000000";
                    when 9 => hex0 <= "0010000";
                    when others => hex0 <= "1111111";
                end case;
            end if;
        end process;
    end
end

```

```

case to_integer(bcdVal(7 downto 4)) is
  when 0 => hex1 <= "1000000";
  when 1 => hex1 <= "1111001";
  when 2 => hex1 <= "0100100";
  when 3 => hex1 <= "0110000";
  when 4 => hex1 <= "0011001";
  when 5 => hex1 <= "0010010";
  when 6 => hex1 <= "0000010";
  when 7 => hex1 <= "1111000";
  when 8 => hex1 <= "0000000";
  when 9 => hex1 <= "0010000";
  when others => hex1 <= "1111111";
end case;

case to_integer(bcdVal(11 downto 8)) is
  when 0 => hex2 <= "1000000";
  when 1 => hex2 <= "1111001";
  when 2 => hex2 <= "0100100";
  when 3 => hex2 <= "0110000";
  when 4 => hex2 <= "0011001";
  when 5 => hex2 <= "0010010";
  when 6 => hex2 <= "0000010";
  when 7 => hex2 <= "1111000";
  when 8 => hex2 <= "0000000";
  when 9 => hex2 <= "0010000";
  when others => hex2 <= "1111111";
end case;

else
  hex0 <= "1111111";
  hex1 <= "1111111";
  hex2 <= "1111111";
end if;
end process;

end behavior;
-----
-----MAIN BLOCK-----

```

The entity of part B takes four inputs, *input_clock*, *reset*, *count_enable*, and *output_enable*. These represent the clock, the reset switch, the incrementation enable switch, and the HEX display activation enable respectively. Three outputs are present, one for each HEX display required.

The architecture of the system begins with defining two signals, one for the clock cycle amount (50 million for a 50MHz clock) and a 12-bit unsigned value initialized as 0. A sensitivity list process begins with two sensitivity parameters, *input_clock* and *restart*. As both inputs present in this system are included in this sensitivity list, the entire system is therefore asynchronous. The first step in the process is to check whether reset is thrown, and if so, both the clock and the BCD value are reset to 0. Otherwise, on any rising edge of the clock, and after a designated number of risen edges, in this case 49,999,999 edges, the clock is reset, and the individual BCD component checking occurs. Then, after the BCD logic, the clock is incremented, the process is ended, and a new process begins with a single parameter sensitivity list containing the *output_enable* input. This process assigns the correct values to each HEX display if the output is enabled, otherwise it

disables all three HEX displays. An issue of note was observed here, that being an attempt to use *with select* statements within a process, which is not possible. Thus, *if case* statements were used to instead drive values to each HEX display conditionally.

Below is the block diagram and pin assignments for this part of the experiment:

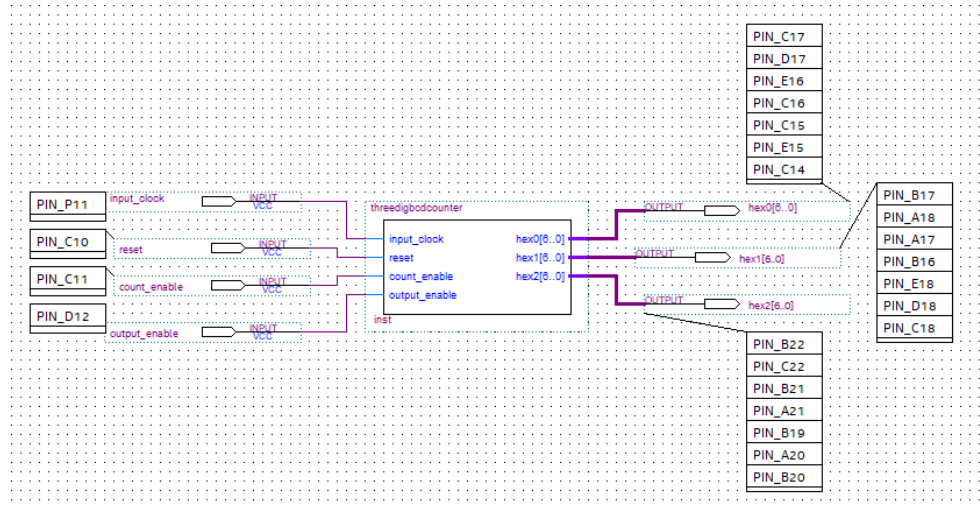


Figure 3 - Part B Block Diagram

in	count_enable	Input	PIN_C11	7	B7_NO	PIN_C11	3.3-V LVTTTL
out	hex0[6]	Output	PIN_C17	7	B7_NO	PIN_C17	3.3-V LVTTTL
out	hex0[5]	Output	PIN_D17	7	B7_NO	PIN_D17	3.3-V LVTTTL
out	hex0[4]	Output	PIN_E16	7	B7_NO	PIN_E16	3.3-V LVTTTL
out	hex0[3]	Output	PIN_C16	7	B7_NO	PIN_C16	3.3-V LVTTTL
out	hex0[2]	Output	PIN_C15	7	B7_NO	PIN_C15	3.3-V LVTTTL
out	hex0[1]	Output	PIN_E15	7	B7_NO	PIN_E15	3.3-V LVTTTL
out	hex0[0]	Output	PIN_C14	7	B7_NO	PIN_C14	3.3-V LVTTTL
out	hex1[6]	Output	PIN_B17	7	B7_NO	PIN_B17	3.3-V LVTTTL
out	hex1[5]	Output	PIN_A18	7	B7_NO	PIN_A18	3.3-V LVTTTL
out	hex1[4]	Output	PIN_A17	7	B7_NO	PIN_A17	3.3-V LVTTTL
out	hex1[3]	Output	PIN_B16	7	B7_NO	PIN_B16	3.3-V LVTTTL
out	hex1[2]	Output	PIN_E18	6	B6_NO	PIN_E18	3.3-V LVTTTL
out	hex1[1]	Output	PIN_D18	6	B6_NO	PIN_D18	3.3-V LVTTTL
out	hex1[0]	Output	PIN_C18	7	B7_NO	PIN_C18	3.3-V LVTTTL
out	hex2[6]	Output	PIN_B22	6	B6_NO	PIN_B22	3.3-V LVTTTL
out	hex2[5]	Output	PIN_C22	6	B6_NO	PIN_C22	3.3-V LVTTTL
out	hex2[4]	Output	PIN_B21	6	B6_NO	PIN_B21	3.3-V LVTTTL
out	hex2[3]	Output	PIN_A21	6	B6_NO	PIN_A21	3.3-V LVTTTL
out	hex2[2]	Output	PIN_B19	7	B7_NO	PIN_B19	3.3-V LVTTTL
out	hex2[1]	Output	PIN_A20	7	B7_NO	PIN_A20	3.3-V LVTTTL
out	hex2[0]	Output	PIN_B20	6	B6_NO	PIN_B20	3.3-V LVTTTL
in	input_clock	Input	PIN_P11	3	B3_NO	PIN_P11	3.3-V LVTTTL
in	output_enable	Input	PIN_D12	7	B7_NO	PIN_D12	3.3-V LVTTTL
in	reset	Input	PIN_C10	7	B7_NO	PIN_C10	3.3-V LVTTTL

Figure 4 - Part B Pin Assignments

Part C – The Real-time Clock

This step of the experiment marks an exciting milestone in this VHDL embedded systems development journey, as it demonstrates the design and implementation of concepts learned to this point in a relatable and useful project, that being creating a functioning real-time clock. This clock will count from 0 to 59 in seconds, then 0 to 59 in minutes subsequently.

Code Explanation Part C

```

12 architecture behavior of realtimeclock is
13
14 signal clk_spread : integer range 0 to 49999999 := 0; -- 50MHz means 50 million cycles per second
15 signal bcdVal : unsigned(15 downto 0) := "0000000000000000"; -- 12-bit BCD value
16
17 begin
18
19   process(input_clock, reset)
20   begin
21     if reset = '1' then
22       clk_spread <= 0;
23       bcdVal <= "0000000000000000";
24     elsif rising_edge(input_clock) then
25       if clk_spread = 49999999 then --once clock reaches 1 second, reset clock and increment BCD
26         clk_spread <= 0;
27         if bcdVal(3 downto 0) = "1001" then --ones seconds stops at 9
28           bcdVal(3 downto 0) <= "0000";
29           if bcdVal(7 downto 4) = "0101" then --tens seconds stops at 6
30             bcdVal(7 downto 4) <= "0000";
31             if bcdVal(11 downto 8) = "1001" then --ones minutes stops at 9
32               bcdVal(11 downto 8) <= "0000";
33               if bcdVal(15 downto 12) = "0101" then --tens minutes stops at 6
34                 bcdVal(15 downto 12) <= "0000"; --reset minutes after 59
35               else
36                 bcdVal(15 downto 12) <= bcdVal(15 downto 12) + "0001"; --increment tens of minutes
37               end if;
38             else
39               bcdVal(11 downto 8) <= bcdVal(11 downto 8) + "0001"; --increment ones of minutes
40             end if;
41           else
42             bcdVal(7 downto 4) <= bcdVal(7 downto 4) + 1; --increment tens of seconds
43           end if;
44         else
45           bcdVal(3 downto 0) <= bcdVal(3 downto 0) + 1; --increment ones of seconds
46         end if;
47       else
48         clk_spread <= clk_spread + 1;
49       end if;
50     end if;
51   end process;
52
53   --hex display conversions
54   with to_integer(bcdVal(3 downto 0)) select --ones seconds
55     hex0 <= "1000000" when 0,
56             "1111001" when 1,
57             "0100100" when 2,
58             "0110000" when 3,
59             "0011001" when 4,
60             "0010010" when 5,
61             "0000010" when 6,
62             "1111000" when 7,
63             "0000000" when 8,
64             "0010000" when 9,
65             "1111111" when others;
66
67   with to_integer(bcdVal(7 downto 4)) select --tens seconds
68     hex1 <= "1000000" when 0,
69             "1111001" when 1,
70             "0100100" when 2,
71             "0110000" when 3,
72             "0011001" when 4,
73             "0010010" when 5,
74             "1111111" when others;
75
76   with to_integer(bcdVal(11 downto 8)) select --ones minutes
77     hex2 <= "1000000" when 0,
78             "1111001" when 1,
79             "0100100" when 2,
80             "0110000" when 3,
81             "0011001" when 4,
82             "0010010" when 5,
83             "0000010" when 6,
84             "1111000" when 7,
85             "0000000" when 8,
86             "0010000" when 9,
87             "1111111" when others;
88
89   with to_integer(bcdVal(15 downto 12)) select --tens minutes
90     hex3 <= "1000000" when 0,
91             "1111001" when 1,
92             "0100100" when 2,
93             "0110000" when 3,
94             "0011001" when 4,
95             "0010010" when 5,
96             "1111111" when others;
97
98 end behavior;

```

Figure 5 - Completed Architecture Block for Section C of the Experiment

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

```

```

entity realtimeclock is
port (
    input_clock, reset : in std_logic;
    hex0, hex1, hex2, hex3 : out std_logic_vector(6 downto 0)
);
end realtimeclock;

```

```

architecture behavior of realtimeclock is

```

```

signal clk_spread : integer range 0 to 49999999 := 0;      -- 50MHz means 50 million cycles per second
signal bcdVal : unsigned(15 downto 0) := "0000000000000000"; -- 12-bit BCD value

```

```

begin
    process(input_clock, reset)
    begin
        if reset = '1' then
            clk_spread <= 0;
            bcdVal <= "0000000000000000";
        elsif rising_edge(input_clock) then
            if clk_spread = 49999999 then --once clock reaches 1 second, reset clock and
increment BCD
                clk_spread <= 0;
                if bcdVal(3 downto 0) = "1001" then --ones seconds stops at 9
                    bcdVal(3 downto 0) <= "0000";
                    if bcdVal(7 downto 4) = "0101" then --tens seconds stops at 6
                        bcdVal(7 downto 4) <= "0000";
                        if bcdVal(11 downto 8) = "1001" then --ones minutes stops at
9
                            bcdVal(11 downto 8) <= "0000";
                            if bcdVal(15 downto 12) = "0101" then --tens
minutes stops at 6
                                bcdVal(15 downto 12) <= "0000"; --reset
minutes after 59
                                    else
                                        bcdVal(15 downto 12) <= bcdVal(15 downto
12) + "0001"; --increment tens of minutes
                                            end if;
                                        else
                                            bcdVal(11 downto 8) <= bcdVal(11 downto 8) +
"0001"; --increment ones of minutes
                                                end if;
                                            else
                                                bcdVal(7 downto 4) <= bcdVal(7 downto 4) + 1; --increment
tens of seconds
                                                    end if;
                                                else
                                                    bcdVal(3 downto 0) <= bcdVal(3 downto 0) + 1; --increment ones of
seconds
                                                        end if;
                                                    else
                                                        clk_spread <= clk_spread + 1;
                                                    end if;
                                                end if;
                                            end process;

--hex display conversions
with to_integer(bcdVal(3 downto 0)) select --ones seconds
    hex0 <= "1000000" when 0,
        "1111001" when 1,
        "0100100" when 2,
        "0110000" when 3,
        "0011001" when 4,
        "0010010" when 5,
        "0000010" when 6,
        "1111000" when 7,
        "0000000" when 8,
        "0010000" when 9,

```

```

                                "1111111" when others;

with to_integer(bcdVal(7 downto 4)) select      --tens seconds
    hex1 <= "1000000" when 0,
        "1111001" when 1,
        "0100100" when 2,
        "0110000" when 3,
        "0011001" when 4,
        "0010010" when 5,
        "1111111" when others;

with to_integer(bcdVal(11 downto 8)) select      --ones minutes
    hex2 <= "1000000" when 0,
        "1111001" when 1,
        "0100100" when 2,
        "0110000" when 3,
        "0011001" when 4,
        "0010010" when 5,
        "0000010" when 6,
        "1111000" when 7,
        "0000000" when 8,
        "0010000" when 9,
        "1111111" when others;

with to_integer(bcdVal(15 downto 12)) select      --tens minutes
    hex3 <= "1000000" when 0,
        "1111001" when 1,
        "0100100" when 2,
        "0110000" when 3,
        "0011001" when 4,
        "0010010" when 5,
        "1111111" when others;

end behavior;

```

The entity portion of this code takes two inputs as *input_clock* and *reset*, with four outputs acting as the HEX display output vectors (representing the ones and tens places of both seconds and minutes)

The architecture of the system begins with defining two signals, one for the clock cycle amount (50 million for a 50MHz clock) and a 16-bit unsigned value initialized as 0. A sensitivity list process begins with two sensitivity parameters, *input_clock* and *restart*. As both inputs present in this system are included in this sensitivity list, the entire system is therefore asynchronous. The first step in the process is to check whether reset is thrown, and if so, both the clock and the BCD value are reset to 0. Otherwise, on any rising edge of the clock, and after a designated number of risen edges, in this case 49,999,999 edges, the clock is reset, and the individual BCD component checking occurs. Then, after the BCD logic, the clock is incremented, the process is ended, and the HEX displays are assigned accordingly using *with select* statements.

Below is the block diagram for the experiment.

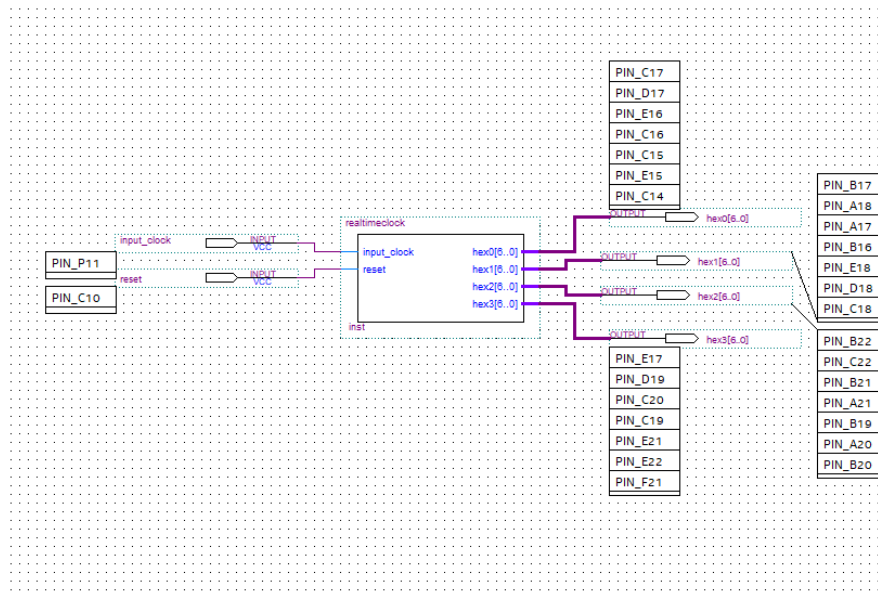


Figure 6 - Part C Block Diagram

out	hex0[6]	Output	PIN_C17	7	B7_NO	PIN_C17	3.3-V LVTTTL
out	hex0[5]	Output	PIN_D17	7	B7_NO	PIN_D17	3.3-V LVTTTL
out	hex0[4]	Output	PIN_E16	7	B7_NO	PIN_E16	3.3-V LVTTTL
out	hex0[3]	Output	PIN_C16	7	B7_NO	PIN_C16	3.3-V LVTTTL
out	hex0[2]	Output	PIN_C15	7	B7_NO	PIN_C15	3.3-V LVTTTL
out	hex0[1]	Output	PIN_E15	7	B7_NO	PIN_E15	3.3-V LVTTTL
out	hex0[0]	Output	PIN_C14	7	B7_NO	PIN_C14	3.3-V LVTTTL
out	hex1[6]	Output	PIN_B17	7	B7_NO	PIN_B17	3.3-V LVTTTL
out	hex1[5]	Output	PIN_A18	7	B7_NO	PIN_A18	3.3-V LVTTTL
out	hex1[4]	Output	PIN_A17	7	B7_NO	PIN_A17	3.3-V LVTTTL
out	hex1[3]	Output	PIN_B16	7	B7_NO	PIN_B16	3.3-V LVTTTL
out	hex1[2]	Output	PIN_E18	6	B6_NO	PIN_E18	3.3-V LVTTTL
out	hex1[1]	Output	PIN_D18	6	B6_NO	PIN_D18	3.3-V LVTTTL
out	hex1[0]	Output	PIN_C18	7	B7_NO	PIN_C18	3.3-V LVTTTL
out	hex2[6]	Output	PIN_B22	6	B6_NO	PIN_B22	3.3-V LVTTTL
out	hex2[5]	Output	PIN_C22	6	B6_NO	PIN_C22	3.3-V LVTTTL
out	hex2[4]	Output	PIN_B21	6	B6_NO	PIN_B21	3.3-V LVTTTL
out	hex2[3]	Output	PIN_A21	6	B6_NO	PIN_A21	3.3-V LVTTTL
out	hex2[2]	Output	PIN_B19	7	B7_NO	PIN_B19	3.3-V LVTTTL
out	hex2[1]	Output	PIN_A20	7	B7_NO	PIN_A20	3.3-V LVTTTL
out	hex2[0]	Output	PIN_B20	6	B6_NO	PIN_B20	3.3-V LVTTTL
out	hex3[6]	Output	PIN_E17	6	B6_NO	PIN_E17	3.3-V LVTTTL
out	hex3[5]	Output	PIN_D19	6	B6_NO	PIN_D19	3.3-V LVTTTL
out	hex3[4]	Output	PIN_C20	6	B6_NO	PIN_C20	3.3-V LVTTTL
out	hex3[3]	Output	PIN_C19	7	B7_NO	PIN_C19	3.3-V LVTTTL
out	hex3[2]	Output	PIN_E21	6	B6_NO	PIN_E21	3.3-V LVTTTL
out	hex3[1]	Output	PIN_E22	6	B6_NO	PIN_E22	3.3-V LVTTTL
out	hex3[0]	Output	PIN_F21	6	B6_NO	PIN_F21	3.3-V LVTTTL
in	input_clock	Input	PIN_P11	3	B3_NO	PIN_P11	3.3-V LVTTTL
in	reset	Input	PIN_C10	7	B7_NO	PIN_C10	3.3-V LVTTTL

Figure 7 - Pin Assignments for Part C

VALIDATION OF DATA

Functional Simulation Analysis

Below is the functional simulation analysis results for Part A, labelled accordingly. Note that these simulations were conducted in Modelsim-Altera.

 


Figure 15 – Correct Incrementation Demonstration

 


Figure 16 – Clear_Bar Throw for Reset

```
# ** Error: Iestbench failed at: 250'0'0'0'
# Time: 38386600 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 260'0'0'0'
# Time: 38386700 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 270'0'0'0'
# Time: 38386800 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 280'0'0'0'
# Time: 38386900 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 290'0'1'1'
# Time: 38387 ns Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 300'0'1'1'
# Time: 38387100 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 310'0'1'1'
# Time: 38387200 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 320'0'1'1'
# Time: 38387300 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 330'0'1'1'
# Time: 38387400 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 340'1'1'0'
# Time: 38387500 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 350'1'1'0'
# Time: 38387600 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 360'1'1'0'
# Time: 38387700 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 370'1'1'0'
# Time: 38387800 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 380'1'1'0'
# Time: 38387900 ps Iteration: 0 Instance: /testbench_eight_bit_counter
# ** Error: Testbench failed at: 390'1'1'1'
```

Figure 17 – Failure cases showing iteration, value, reset state, enable state

CONCLUSION

The study was conducted successfully and efficiently demonstrated three different projects each following their own unique concept, with a shared idea of using a clock-based system. The first section of the study demonstrated the creation of a testbench for a clock-based system created in a previous study. This required the generation of an artificial clock, and testing against numerous

types of failure cases using an iterative approach to ensure a broad range of testing scenarios. The second component to the experiment transitioned to designing a 3-digit BCD counter, which would aid in the design of part C of the study. This part B focused on using a single BCD value to increment three different HEX displays, each counting to 9 then overflowing back to 0, incrementing the next display subsequently. Finally, the third and final part of the experiment designed a real-time clock which counted up to an hour in minutes and seconds. A similar approach to part B was used to complete this task, using a single BCD value to increment selectively increment through to values assigned to each HEX display. If this experiment were to be conducted again, testbenches could be created for each section of the lab, an additional digit could be added to the counter in part B or a structural approach used instead of behavioral, and finally an additional milliseconds component could be implemented into part C.

REFERENCES

[1] Professor Ashley Evans, *Logic Devices Programming Lab Manual*, 1st ed. Orlando, FL. Valencia College, 2025.